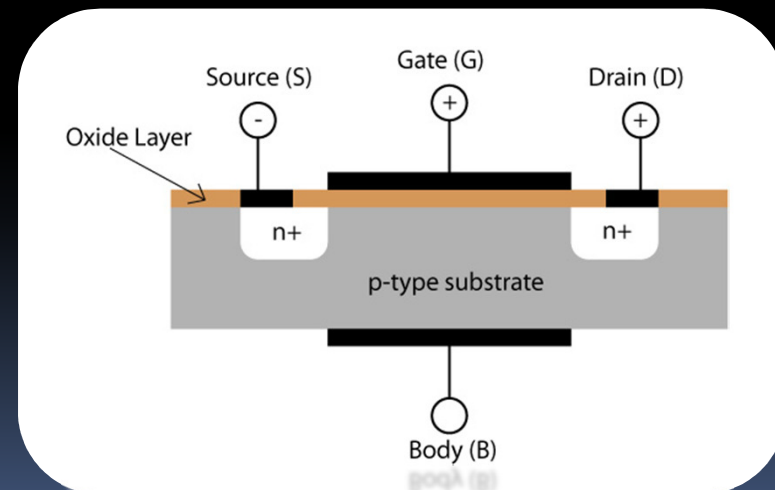


# Quiz 2


# Week 1 Review

- Properties of electricity
- Semiconductor materials
  - Doping (n-type and p-type)
- p-n junctions
- Transistors
  - MOSFETs


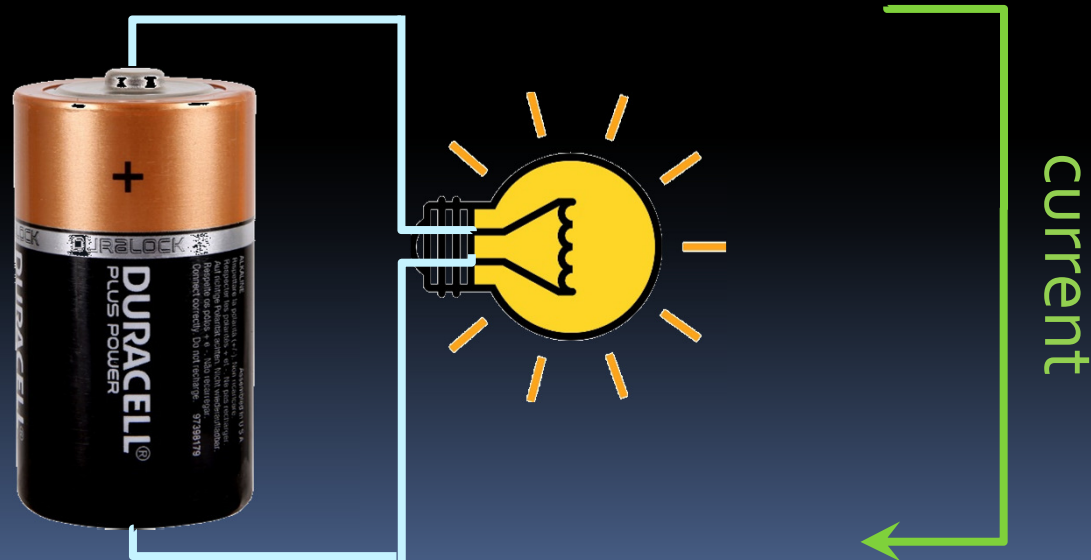
# Electricity review

- If electrons are traveling from the bottom of the battery to the top, which way is current said to be traveling?
  - Current is measured as the movement of **positive charges**.



# Transistor review

- Logic gates are built from transistors



This transistor is called nMOS

It conducts (i.e., acts as a closed switch) if we apply 5 Volts (logic-1) at its gate.




This transistor is called pMOS

It conducts (i.e., acts as a closed switch, if we apply 0 Volts (logic-0, Gnd) at its gate.

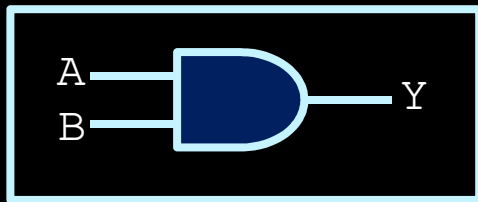
# Basic Logic Gates: Symbols and Truth Tables

- What are the names and truth table values for the following gates?


How many transistors do you need to build a NOT gate?



A	B	Y
0	0	
0	1	
1	0	
1	1	

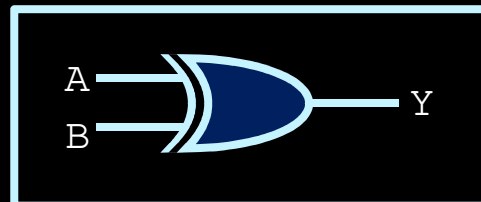


A	B	Y
0	0	
0	1	
1	0	
1	1	

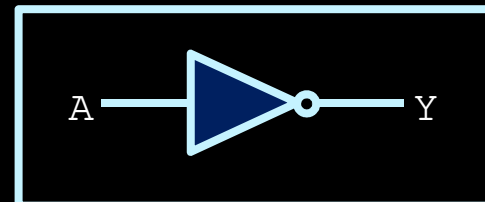


A	Y
0	
1	
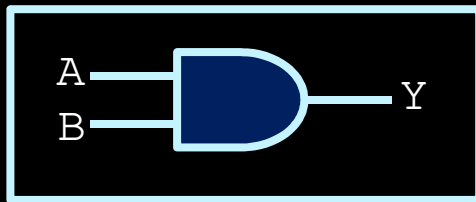
# Basic Logic Gates: Symbols and Truth Tables


- What are the names and truth table values for the following gates?



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

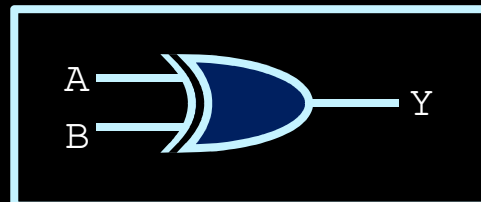


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

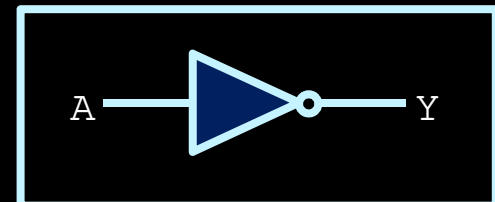

A	Y
0	1
1	0

# Question 1: Which gate is this one?

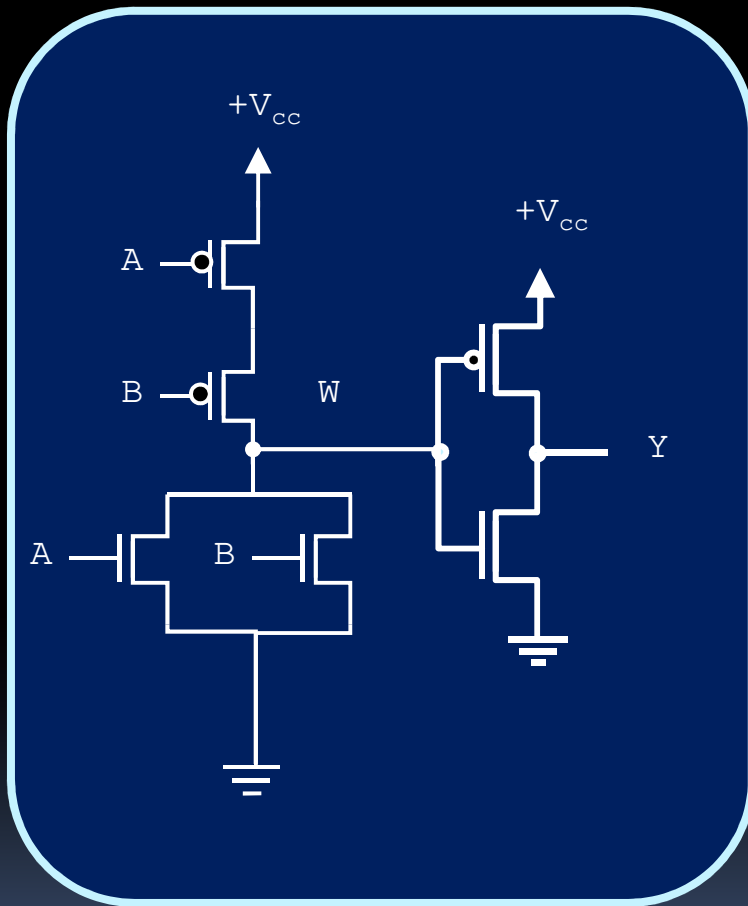


A	B	W	Y
0	0		
0	1		
1	0		
1	1		

$$W = \boxed{\phantom{00}}$$

$$Y = \boxed{\phantom{00}}$$

# Which gate is this one?

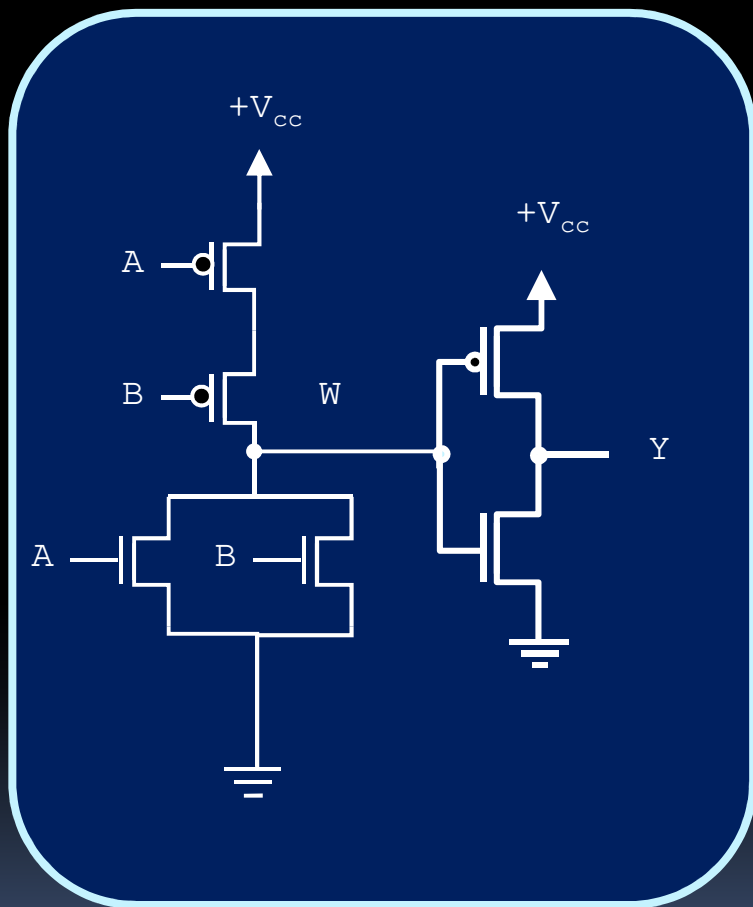

A	B	W	Y
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1


$$W = \overline{(A + B)}$$

$$Y = (A + B)$$


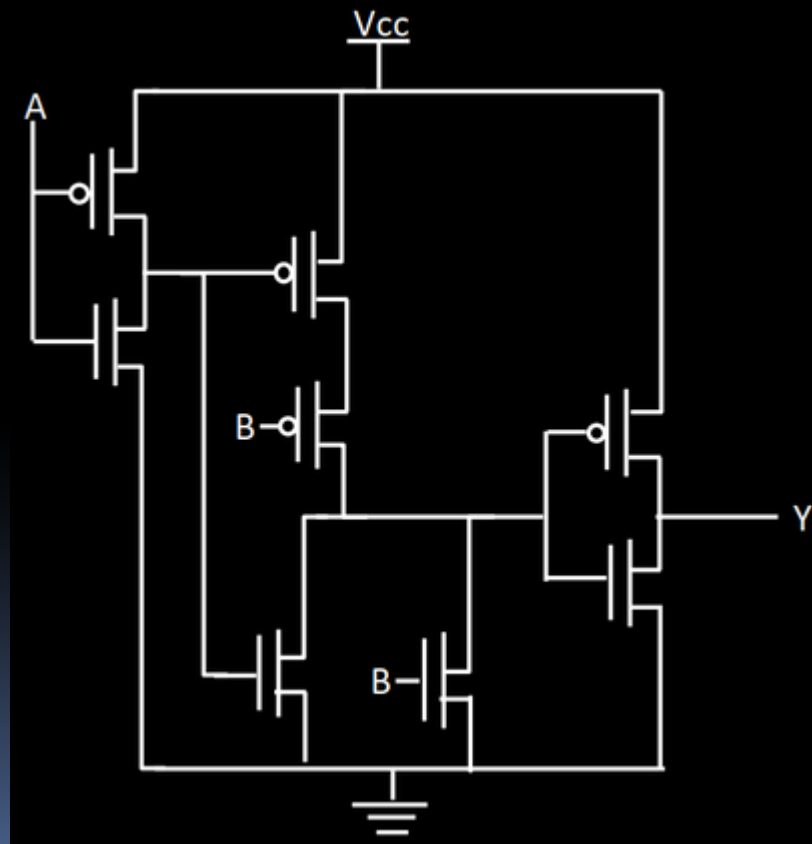
## Question 2

State the following output Y's Boolean expression in terms of A and B:



A	B	Y
0	0	1
0	1	1
1	0	0
1	1	1

Ans:  $Y = A' + B$

## Question 4

True or False? Doping gives a semiconductor an overall positive or negative charge.

Ans: False

## Question 5

What kind of bias on a pn junction causes the depletion layer to expand?

**Ans: Reverse Bias**


## Question 6



Phosphorus has 5 electrons in its outer valence shell. When added in small amounts to silicon, the result is a \_\_\_\_\_ semiconductor.

Ans: N-type

# Question 7

- What gate is created by the following?

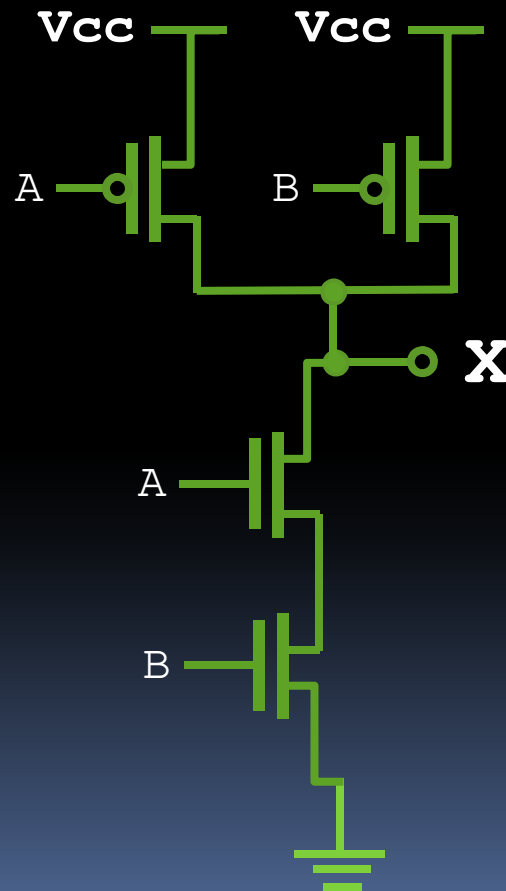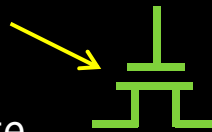


Remember: transistors that look like  are activated when the gate input is high, whereas transistors that look like  are activated when the gate input is low.

Ans:  $X = A \text{ NAND } B$
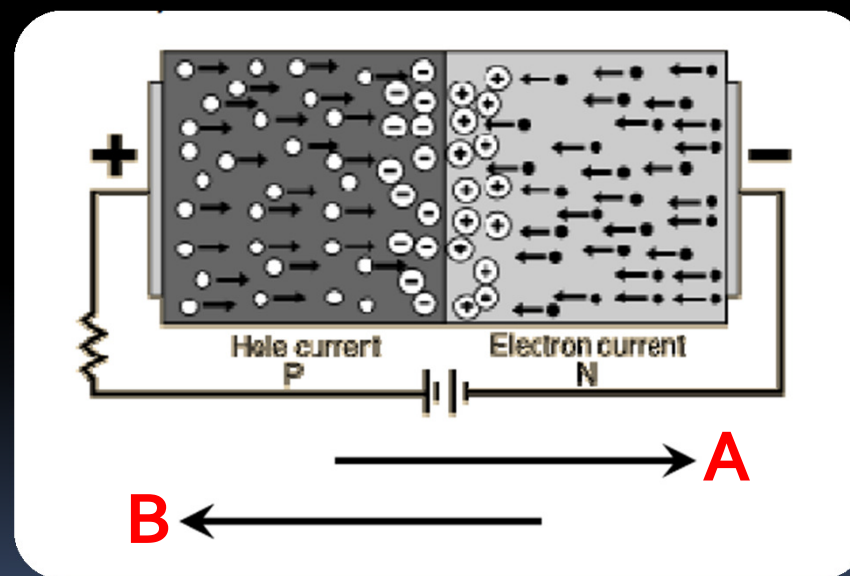
# Question 8


- What is the name of currents A and B, and how are they produced?


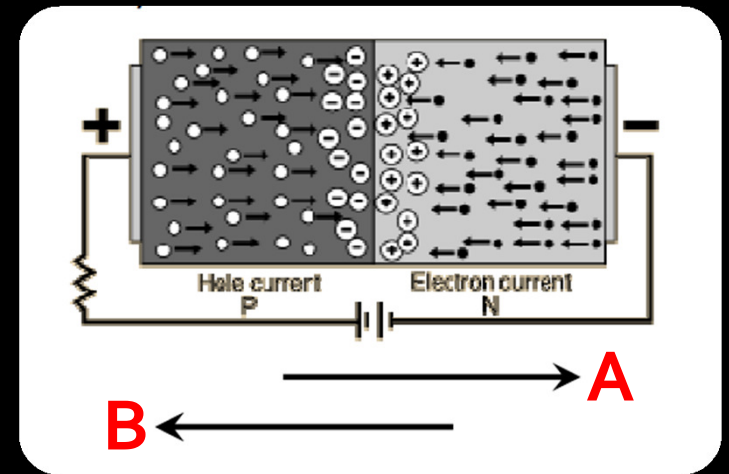
# Kinds of current

- Two things to note here:

- Need to determine which electrons are moving from high concentration to low concentration (**diffusion**), and which are moving because of the electric field (**drift**).
- Remember: Current is measured in the opposite direction of electron flow (i.e. as *the flow of positive charge* through the material)
- **A** → diffusion      **B** → drift






# Group Questions & Answers




# Question 1

- How can you express a two-input XOR gate as a combination of NAND and NOT gates?
  - Draw the circuit using only these two logic gates.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

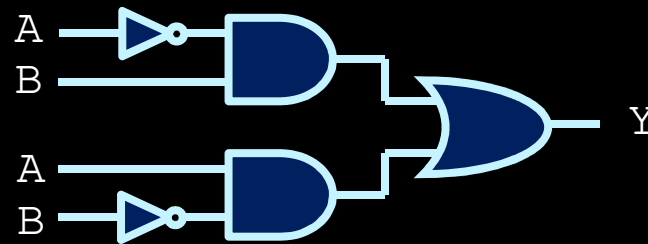

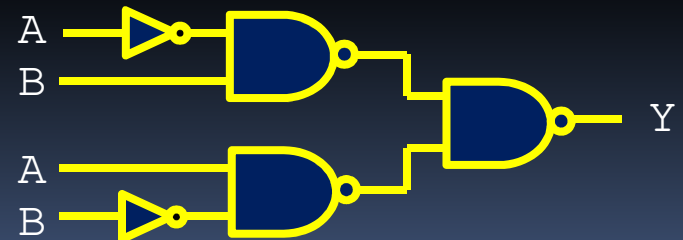- Remember De Morgan's!
  - $(\overline{W} + \overline{Z}) = \overline{(\overline{W} \overline{Z})}$



## Question 2

- What is the most reduced form, in sum of products form, of the function from the truth table on the right?

$$Y = m_0 + m_1 + m_2 + m_5 + m_7 + m_8 + m_9 + m_{10} + m_{13} + m_{15}$$

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

## Question 2 (cont'd)

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	1	0	1
$\bar{A} \cdot B$	0	1	1	0
$A \cdot B$	0	1	1	0
$A \cdot \bar{B}$	1	1	0	1

$$Y = \bar{C} \cdot D + B \cdot D + \bar{B} \cdot \bar{D}$$

## Question 2 (alternative)

- An alternative grouping:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	1	0	1
$\bar{A} \cdot B$	0	1	1	0
$A \cdot B$	0	1	1	0
$A \cdot \bar{B}$	1	1	0	1

$$Y = \bar{B} \cdot \bar{C} + B \cdot D + \bar{B} \cdot \bar{D}$$


# Helpful Hint

AB \ CD		C			
		00	01	11	10
A	00	1	1	0	1
	01	0	1	1	0
	11	0	1	1	0
	10	1	1	0	1

Diagram illustrating a 4x4 Karnaugh map with groupings:

- Group A: Rows 11 and 10 (AB).
- Group B: Columns 11 and 10 (CD).
- Group C: Columns 11 and 10 (CD).
- Group D: Columns 11 and 10 (CD).

# Question 3

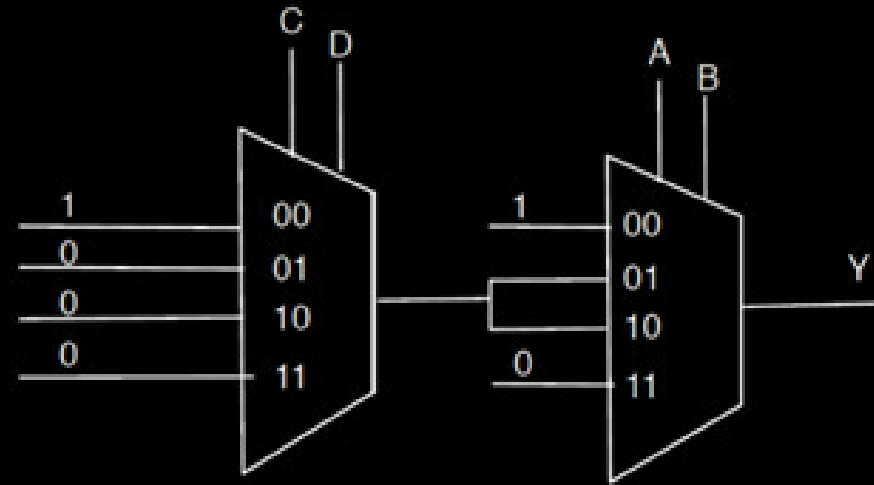

C	D	Y
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Y
0	0	1
0	1	X
1	0	X
1	1	0

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	1	1	1
$\bar{A} \cdot B$	1	0	0	0
$A \cdot B$	0	0	0	0
$A \cdot \bar{B}$	1	0	0	0

$$Y = \underline{A'B'} + A'C'D' + B'C'D'$$