 




Week 2 & 3 Review

Review of past lecture:

- Last week we learned:
- Using logic gates
 - Combinational circuits
 - Circuit reduction
 - Karnaugh maps
- Logical Devices
 - Multiplexer
 - Decoder
 - Adder/Subtractor
 - Comparator






Gate Conversions



Quiz 3

Question 1

- How can you implement a NOT gate from a 2-input NAND gate?

   

Question 2 - Minterms

- Write Y in SOM (Sum Of Minterms) form.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C$$

$$Y = m_1 + m_2 + m_4 + m_7$$

Question 3 - Maxterms

- Write Y in POM (Product Of Maxterms) form.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = \overline{A+B+C} \cdot \overline{A+B+C} \cdot \overline{A+B+C} \cdot \overline{A+B+C}$$

$$Y = M_0 \cdot M_3 \cdot M_5 \cdot M_6$$

Question 4

Given the Karnaugh map on the right for an output called Y , what is the equation for **the most reduced form** of this circuit.

$$Y = B' + D'$$

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	1	1	1

Question 5

Given the Karnaugh map on the right for an output called Y:

a. Gate Cost: 1

b. Gate Cost (including NOTs)

: 3

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	1	1	1

Practice Question

- Given the minterms below, can you fill in the truth table on the right?

$$Y = m_2 + m_3 + m_7 + m_9 + m_{12} + m_{14}$$

A	B	C	D	Y
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Practice Question

- Given the minterms below, can you fill in the truth table on the right?

$$Y = m_2 + m_3 + m_7 + m_9 + m_{12} + m_{14}$$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Question 6-8

6. How do you write the number 78 as an 8-bit binary number?

128	64	32	16	8	4	2	1
0	1	0	0	1	1	1	0

7. What is the two's complement of 01101101?

10010011

← Tip for 2's comp:
preserve the first '1' and invert

8. What is the sum of 01101101 and 01101101?

11011010

← Note what's
happening here!

Question 9

- What groupings are in the K-map on the right?


	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	1	X	1
$A \cdot \bar{B}$	X	0	X	1
$A \cdot B$	1	X	X	1
$\bar{A} \cdot B$	1	X	0	X

- What logic equations do these groupings represent?

$$\bar{A} \cdot \bar{B} + \bar{D}$$

 Question 10

Which Row is the forbidden state for this circuit?



Row	\overline{S}	\overline{R}	Q_T	\overline{Q}_T	Q_{T+1}	\overline{Q}_{T+1}
A	0	0	X	X	1	1
B	0	1	X	X	1	0
C	1	0	X	X	0	1
D	1	1	0	1	0	1
E	1	1	1	0	1	0


Row A



Group Questions

 Question 1

What is the Sum of Minterms equation for the circuit shown below:





$$F = m_0 + m_1 + m_2 + m_4 + m_5$$

$$F = \sum m(0,1,2,4,5)$$


Question 2

- How would you implement the $A==B$ output of the 2-bit comparator below out of 1-bit comparators and a minimal number of gates?

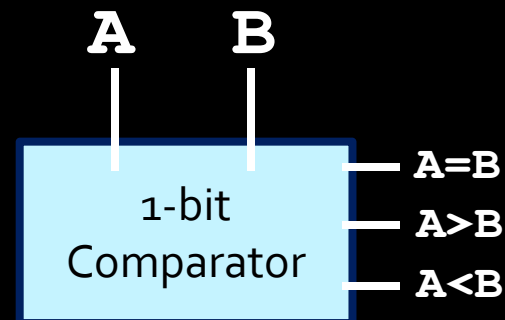 

Question 2 - Answer

- The implementation of the $A==B$ signal:

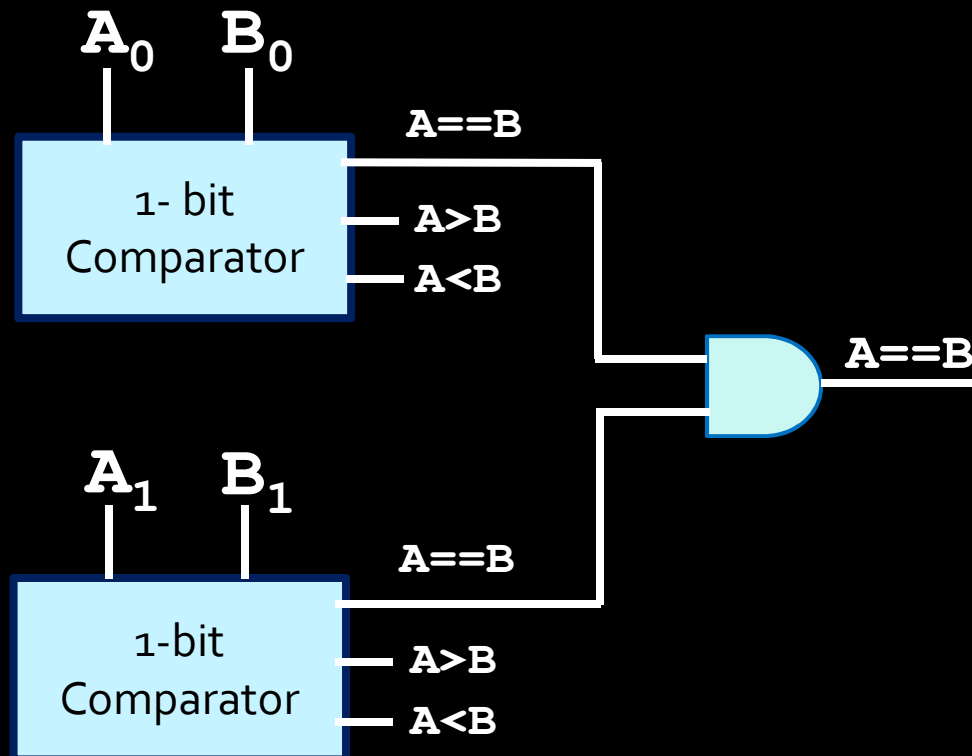

Question 3

- How would you implement the $A > B$ output of the 2-bit comparator below out of 1-bit comparators and a minimal number of gates?

