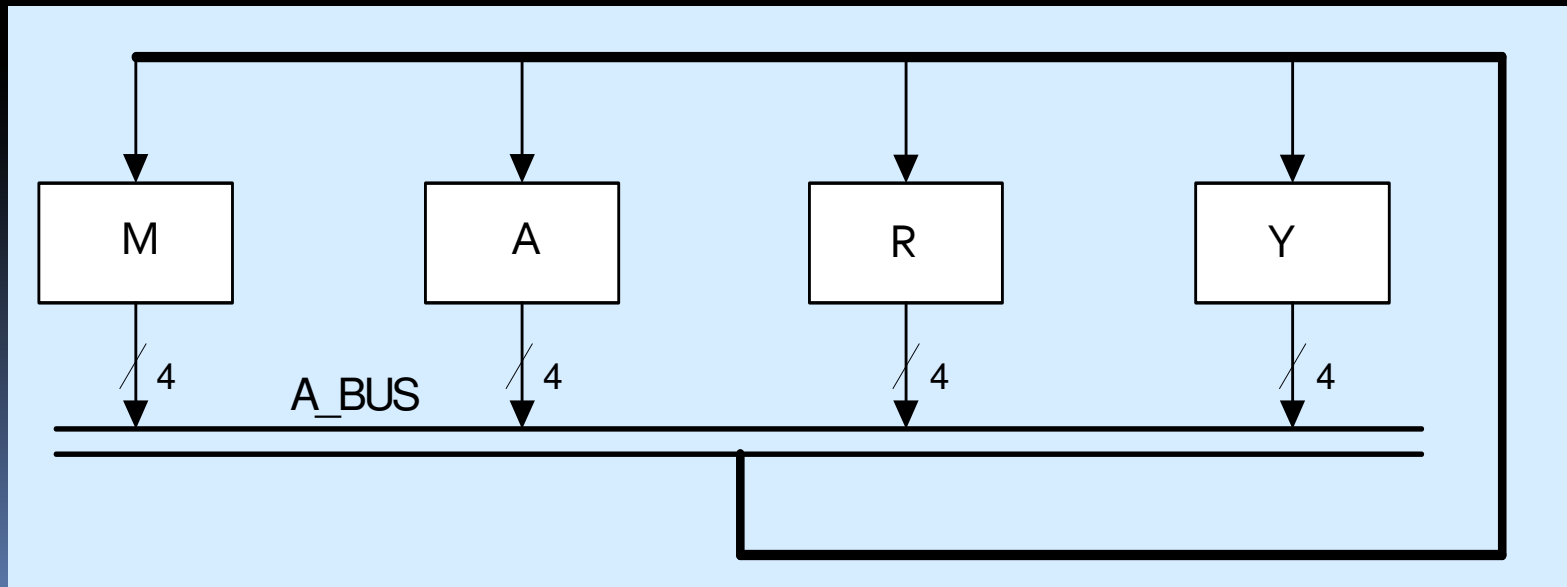





# Week 6 Review

# FSM Example


- A data bus, labeled A\_BUS, is used to create a shared data routing path between four 4-bit registers, M, A, R and Y.
  - 1) How would you implement this data bus using the combinational/sequential devices that you have learned so far?
  - 2) What control signals are needed in your design (i.e. clock)?



# Using multiplexors

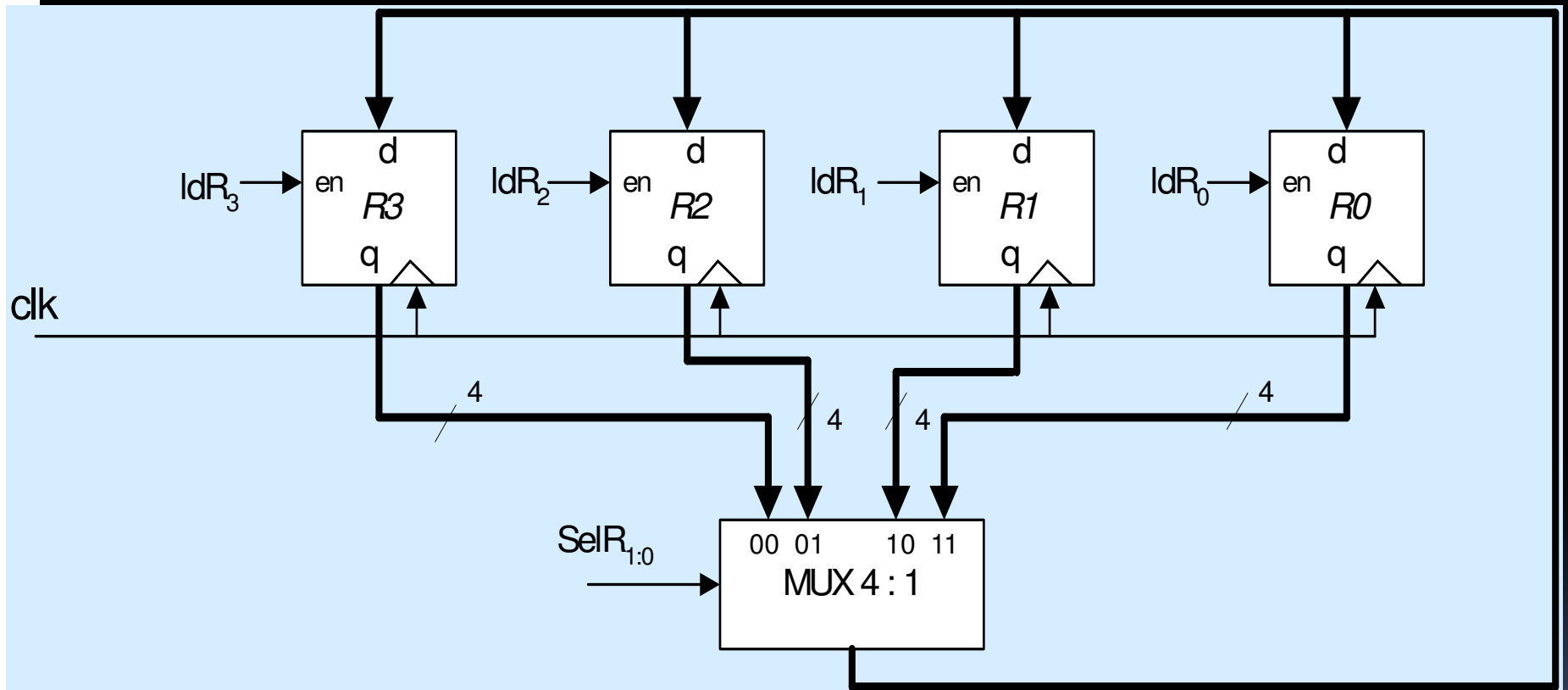

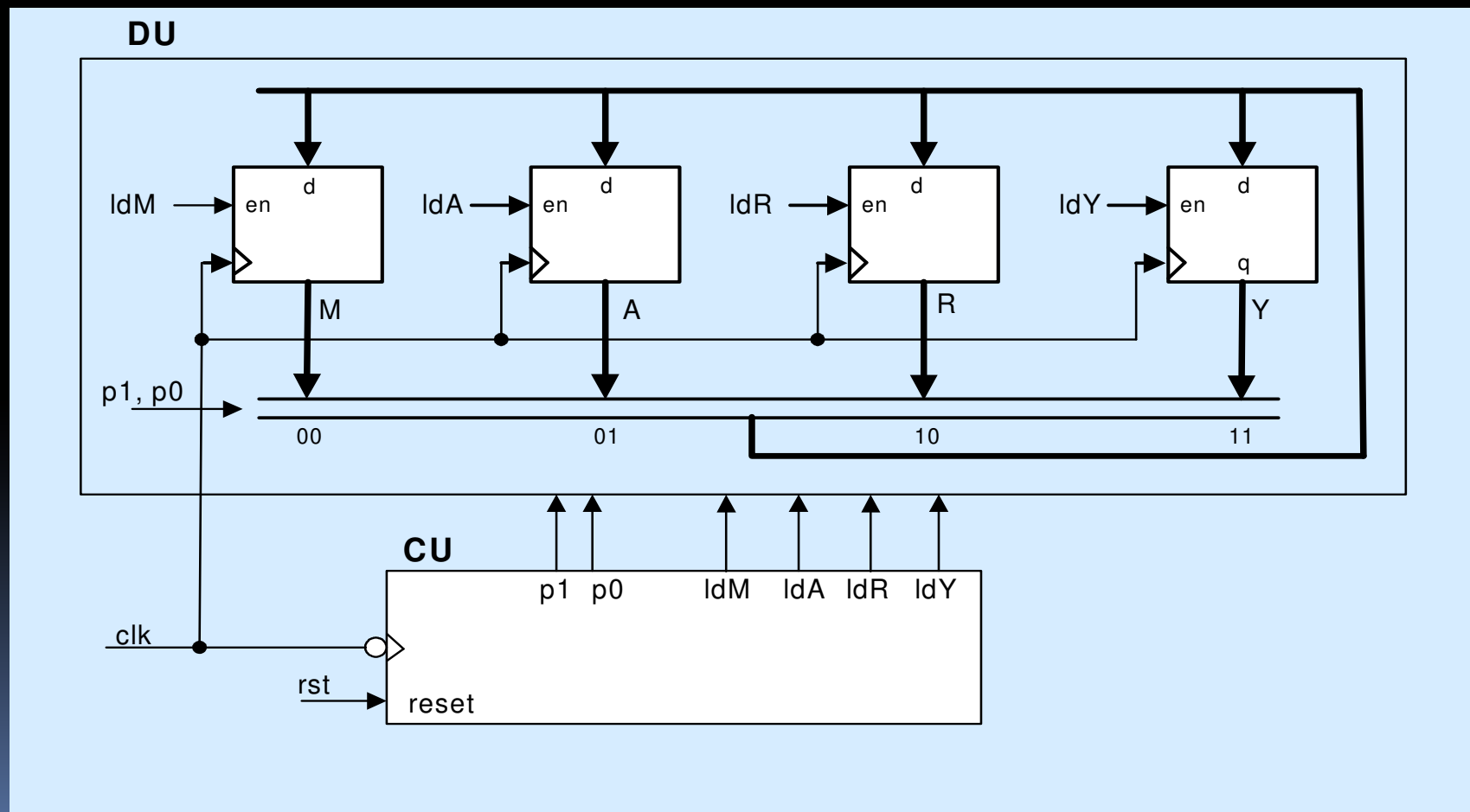
- Datapath Unit (DPU or DU)
- Control Unit



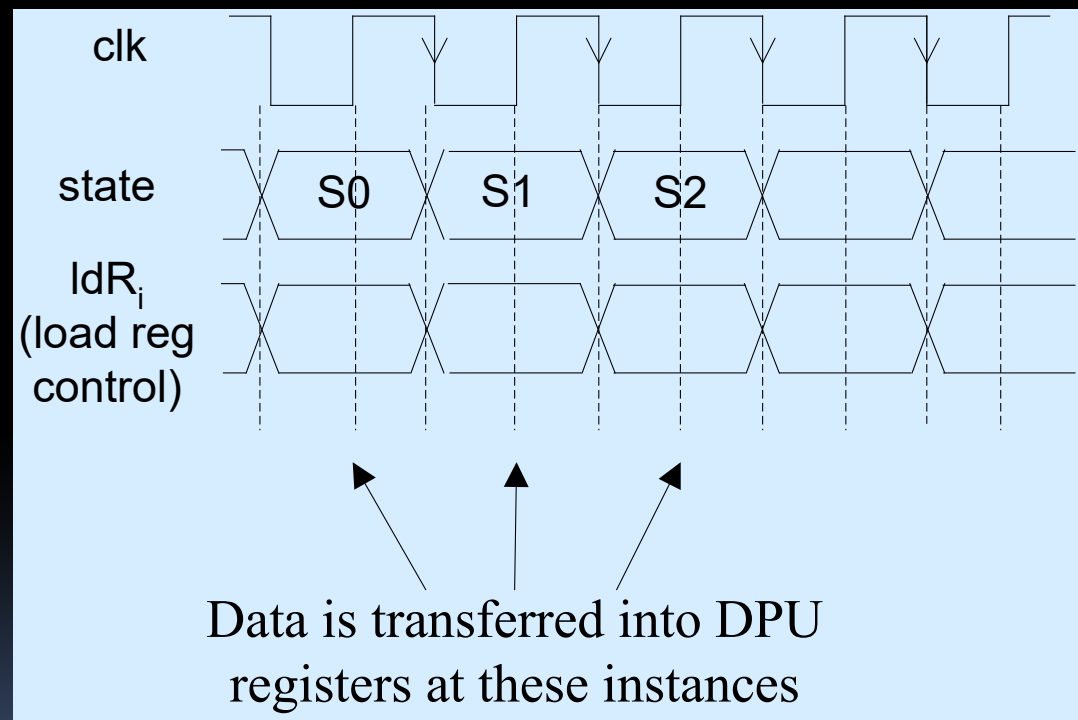
# Data Bus Example

- The following process needs to be implemented:

- $S_0$  :  $M \leftarrow A$
- $S_1$  :  $A \leftarrow Y$
- $S_2$  :  $R \leftarrow M$
- $S_3$  :  $Y \leftarrow R,$   
 $M \leftarrow R$


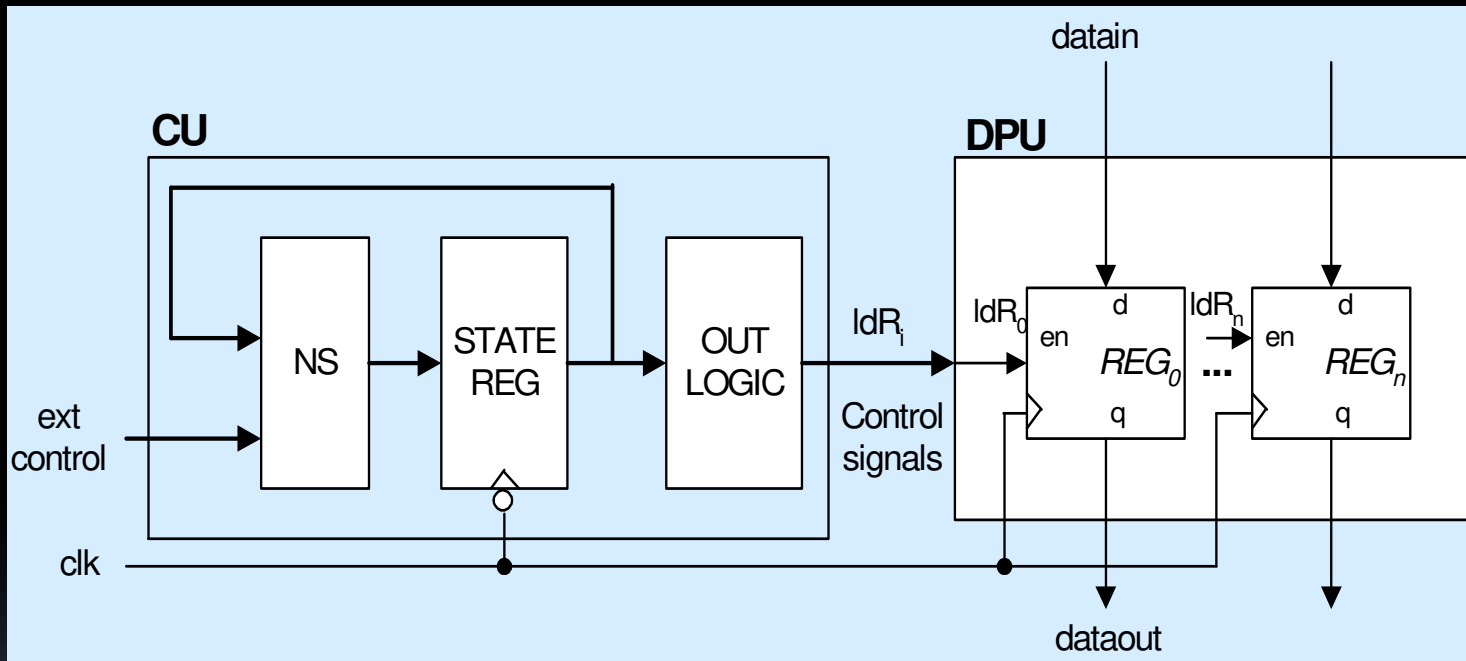
# Control Unit (CU) and Datapath Unit (DU)



# Data Bus Example

RTL operations	Control Vector [p <sub>1</sub> p <sub>0</sub> ldM ldA ldR ldY]
S <sub>0</sub> :M ← A	
S <sub>1</sub> :A ← Y	
S <sub>2</sub> :R ← M	
S <sub>3</sub> :Y ← R, M ← R ()/goto S <sub>0</sub> .	

# Data Bus Example


RTL operations	Control Vector [p <sub>1</sub> p <sub>0</sub> ldM ldA ldR ldY]
S <sub>0</sub> :M ← A	0 1 1 0 0 0 (18Hex)
S <sub>1</sub> :A ← Y	1 1 0 1 0 0 (34Hex)
S <sub>2</sub> :R ← M	0 0 0 0 1 0 (02Hex)
S <sub>3</sub> :Y ← R, M ← R (/goto S <sub>0</sub> .)	1 0 1 0 0 1 (29Hex)



# Quiz 5
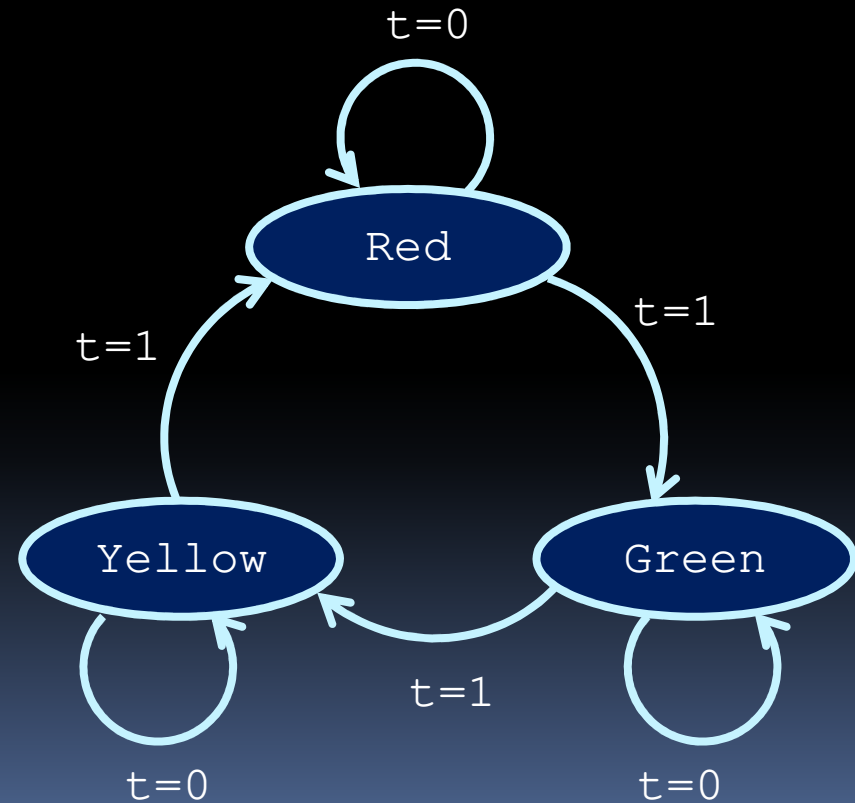
# Question 1: Traffic Light

Complete the state table for the FSM represented by the following state diagram:



# Question 1

Output, Color changer (CC):

- 00 => Red color,
- 01 => Green color,
- 10 => Yellow color

Current state	t	Next State	CC
Red	0	Red	00
Red	1	Green	01
Green	0	Green	01
Green	1	Yellow	10
Yellow	0	Yellow	10
Yellow	1	Red	00

## Question 2:

- What is the equation for  $F_1^*$ ?
- Hint: use CC as your state variable.

	$\overline{F_0} \cdot \overline{t}$	$\overline{F_0} \cdot t$	$F_0 \cdot t$	$F_0 \cdot \overline{t}$
$\overline{F_1}$	0	0	1	0
$F_1$	1	0	X	X

$$F_1^* = F_0.t + F_1.t'$$

## Question 3:


- What is the equation for  $F_o^*$ ?

	$\bar{F}_0 \cdot \bar{t}$	$\bar{F}_0 \cdot t$	$F_0 \cdot t$	$F_0 \cdot \bar{t}$
$\bar{F}_1$	0	1	0	1
$F_1$	0	0	X	X

$$F_o^* = F_o \cdot t' + F_1' \cdot F_o' \cdot t$$


# Question 4:

- Draw your FSM circuit diagram?

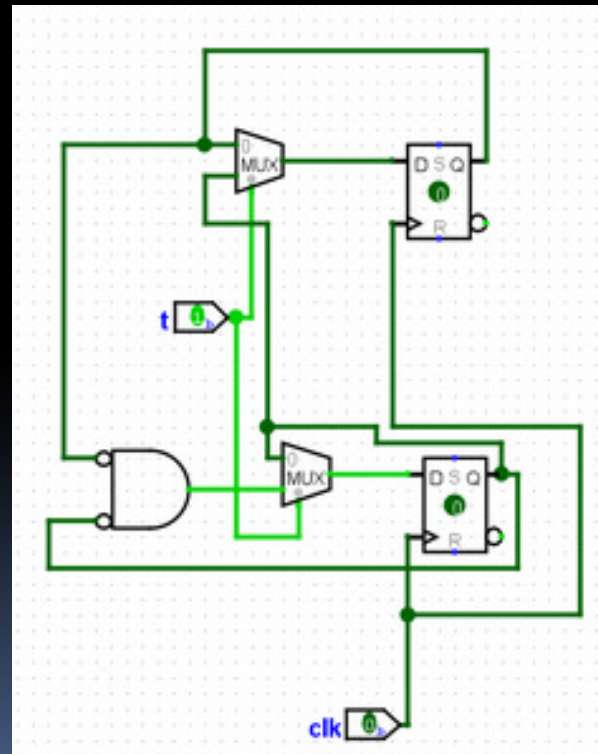
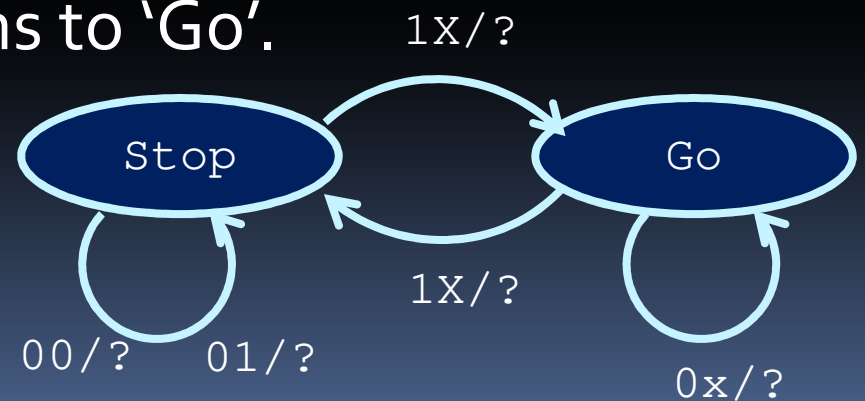
# Question 5: Pedestrian Crossing

The pedestrian crossing is a Mealy machine and is an add-on to the traffic light. Other than the first input timer (t), it has a secondary input, p which is the signal generated when a pedestrian presses the button indicating they would like to cross the road. This produces an output Z which will be used to speed-up the timer that will cause the traffic light to turn Red for cars and allow the pedestrians to 'Go'.



## Question 6:

- What is the equation for  $F_o^*$  for the pedestrian signal?

	$\bar{t} \cdot \bar{p}$	$\bar{t} \cdot p$	$t \cdot p$	$t \cdot \bar{p}$
$\bar{F}_0$	0	0	1	1
$F_0$	1	1	0	0

$$F_o^* = F_o't + Fot'$$



# Question 7:

- Draw your FSM circuit diagram?

